


Ranken Technical College

Name _____

Date _____ Class _____

From the scope drawings determine the following values


Time/cm 20 μ s
Volt/cm 50mV

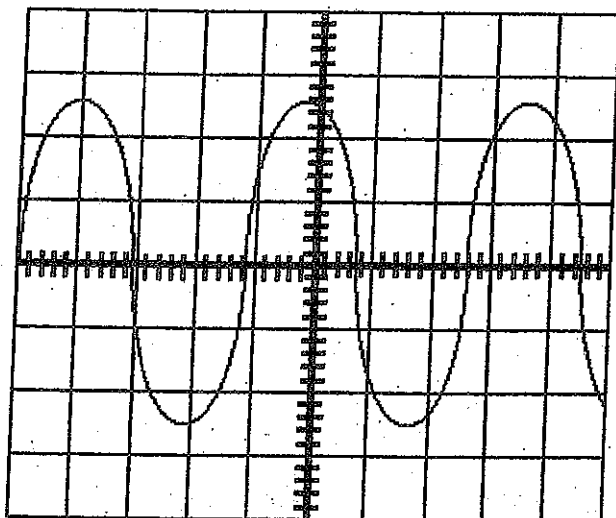


time _____ frequency _____ Vpp _____ Vp _____ Vrms _____

Name _____ Date _____ Class _____

lab\phase1

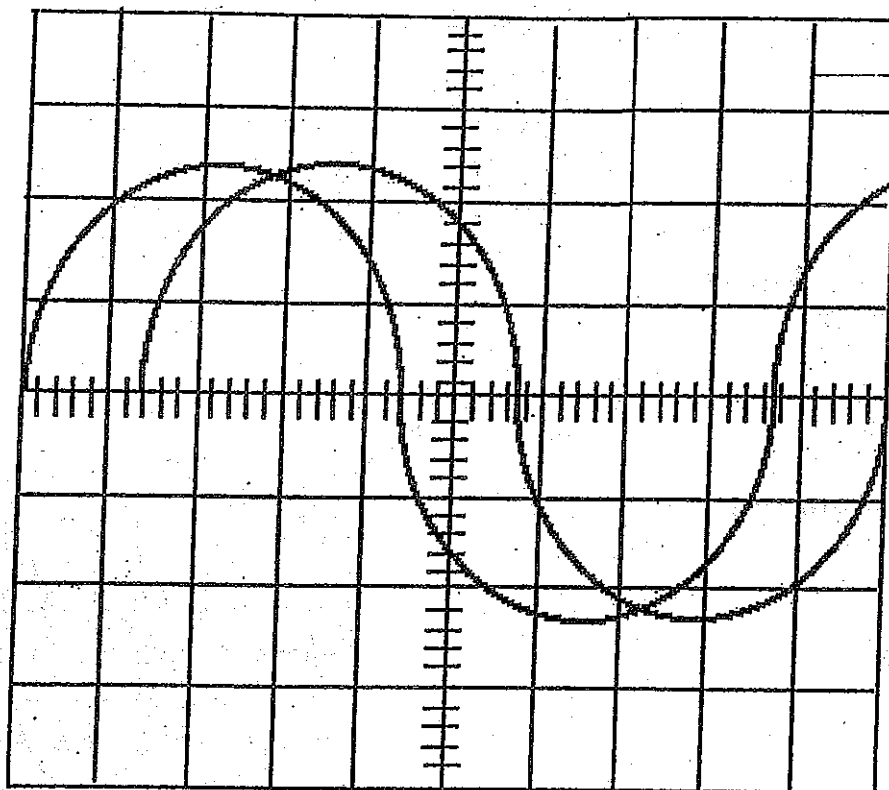

Phase Angle = _____ degrees.

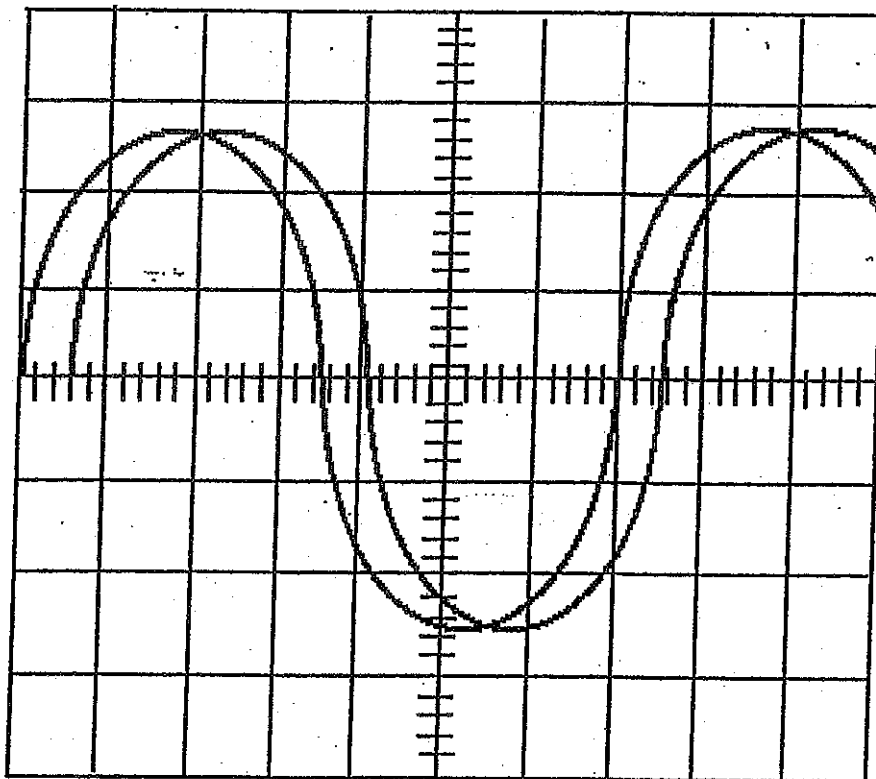


Phase Angle = _____ degrees.

Duty C Troubleshooting 1

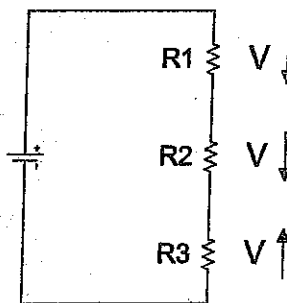
1. From the drawing below answer the following questions

- Total current increase / decrease
- What is the malfunction open / short
- Define the malfunction _____
- Knowing the type of malfunction, what will the voltage drops do across the components that do not have a change in resistance increase / decrease
- Which component's voltage does not follow the criteria in step D. R1 R2 R3



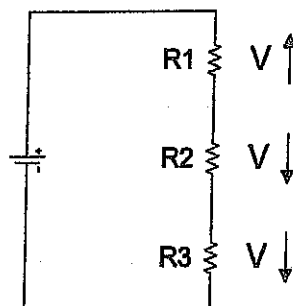2. From the drawing below answer the following questions


- Total current increase / decrease
- What is the malfunction open / short
- Define the malfunction _____
- Knowing the type of malfunction, what will the voltage drops do across the components that do not have a change in resistance increase / decrease
- Which component's voltage does not follow the criteria in step D. R1 R2 R3



Duty C Troubleshooting 1

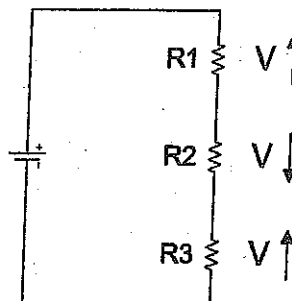
3. From the drawing below answer the following questions

- Total current increase / decrease
- What is the malfunction open / short
- Define the malfunction _____
- Knowing the type of malfunction, what will the voltage drops do across the components that do not have a change in resistance increase / decrease
- Which component's voltage does not follow the criteria in step D. R1 R2 R3



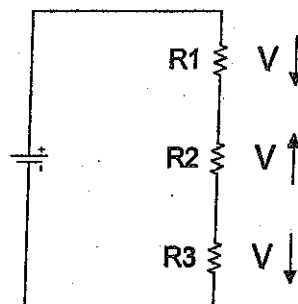4. From the drawing below answer the following questions


- Total current increase / decrease
- What is the malfunction open / short
- Define the malfunction _____
- Knowing the type of malfunction, what will the voltage drops do across the components that do not have a change in resistance increase / decrease
- Which component's voltage does not follow the criteria in step D. R1 R2 R3



Duty C Troubleshooting 1

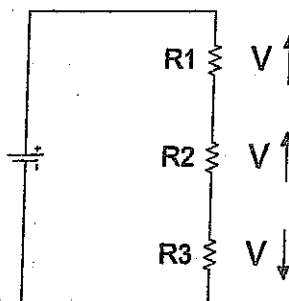
5. From the drawing below answer the following questions

- Total current increase / decrease
- What is the malfunction open / short
- Define the malfunction _____
- Knowing the type of malfunction, what will the voltage drops do across the components that do not have a change in resistance increase / decrease
- Which component's voltage does not follow the criteria in step D. R1 R2 R3



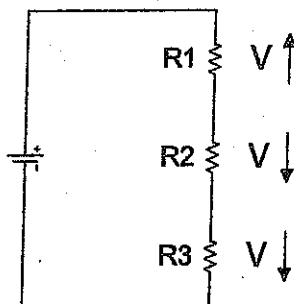6. From the drawing below answer the following questions

- Total current increase / decrease
- What is the malfunction open / short
- Define the malfunction _____
- Knowing the type of malfunction, what will the voltage drops do across the components that do not have a change in resistance increase / decrease
- Which component's voltage does not follow the criteria in step D. R1 R2 R3



Name _____
Date _____ Class _____

1. Band 1 - Green
Band 2 - Yellow
Band 3 - Brown
Band 4 - None

Resistor Value = _____
Tolerance in % = _____
Tolerance in Ohms = _____
Maximum Resistor Value = _____
Minimum Resistor Value = _____

2. Band 1 - Brown
Band 2 - Black
Band 3 - Orange
Band 4 - Silver

Resistor Value = _____
Tolerance in % = _____
Tolerance in Ohms = _____
Maximum Resistor Value = _____
Minimum Resistor Value = _____

3. Band 1 - Gray
Band 2 - Red
Band 3 - Silver
Band 4 - Gold

Resistor Value = _____
Tolerance in % = _____
Tolerance in Ohms = _____
Maximum Resistor Value = _____
Minimum Resistor Value = _____

4. Band 1 - Violet
Band 2 - Blue
Band 3 - Gold
Band 4 - Silver

Resistor Value = _____
Tolerance in % = _____
Tolerance in Ohms = _____
Maximum Resistor Value = _____
Minimum Resistor Value = _____

5. Band 1 - Blue
Band 2 - Brown
Band 3 - Yellow
Band 4 - None

Resistor Value = _____
Tolerance in % = _____
Tolerance in Ohms = _____
Maximum Resistor Value = _____
Minimum Resistor Value = _____

Ranken Technical College

General Knowledge Lab quiz

1. In a series circuit voltage adds, current adds and resistance adds.

True or False

2. In a parallel circuit branch current adds, Voltage stays the same and if another branch is added the total resistance will go down.

True or False

3. In a series circuit if another resistor is added to the circuit the total resistance will go up. Therefore the circuit current will.

A. Go up

B. Go down

4. In a Inductive circuit it is said that there is a phase shift between current and voltage across the resistor.

True or False

5. In a Capacitive circuit it is said that there is no phase shift between current and voltage across the resistor.

True or False

6. In a Inductive circuit across the inductor there is a phase shift the current will lead the voltage.

True or False

7. In a Capacitive circuit across the Capacitor there is a phase shift the current will lead the voltage.

True or False

8. A(n) open can best be defined as a increase in resistance therefore a decrease in current.

True or False

9. A(n) short can best be defined as a increase in resistance therefore a decrease in current.

True or False

10. When reading voltage across a(n) OPEN or an open switch you should read source voltage.

True or False


From the drawing answer the following questions:

11. Total current.

- A. increase
- B. decrease

12. What is the malfunction

- A. open
- B. short

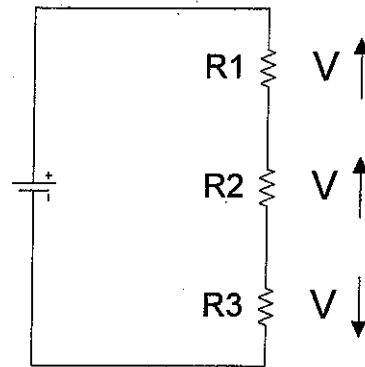

13. Is the resistance of R1 & R2 going down causing the voltage to rise on R1 & R2 .

- A. Yes
- B. No

14. Knowing the type of malfunction, what will the voltage drops do across Resistors R1 & R2 (that do not have a change in resistance).

- A. increase
- B. decrease

15. Which resistor has the malfunction.
- A. R1
 - B. R2
 - C. R3
16. When capacitors are placed in a series the capacitance will add to solve for total capacitance.
- A. True
 - B. False
17. When capacitors placed in a parallel circuit the capacitance will add like resistors do in a series circuit.
- A. True
 - B. False
18. When inductors are placed in series you must use the reciprocal method to solve for total inductance.
- A. True
 - B. False
19. In a series circuit voltage adds, current stays the same and resistance adds.
- A. True
 - B. False
20. In a series circuit if another resistor is added to the circuit and the power supply is set to (10V) The circuit total current will ?
- A. Go down
 - B. Go up